

ESP32-S3 Meter Coupler - Simplified Section-by-Section Schematics

PART 1: POWER SUPPLY (Start Here!)

This is the simplest part. Just 4 steps:

Step 1: Connect Battery

Red wire (Battery +) —► to ONE side of switch

Black wire (Battery -) —► to GND rail

Step 2: Connect Switch

Other side of switch —► to AMS1117 regulator VIN pin

Step 3: Connect Regulator (AMS1117-3.3)


VIN (pin 1) ◀— from switch

GND (pin 2) —► to GND rail (black wires)


OUT (pin 3) —► to +3.3V rail

Step 4: Add Capacitors (these keep voltage clean)


Input side (between VIN and GND):

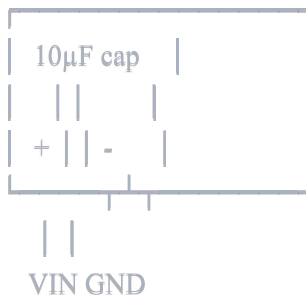

Output side (between OUT and GND):

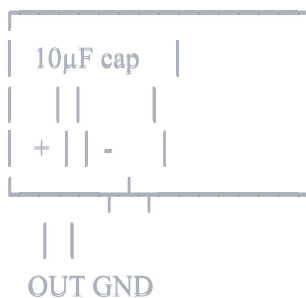

Big cap on output (bulk filtering):

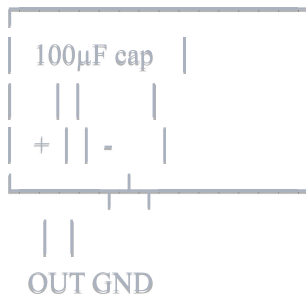


RESULT: You now have clean 3.3V power for everything!

PART 2: LED INDICATORS (Very Simple!)

There are 3 LEDs. Each one is identical:

LED #1: GREEN (Power On Indicator)

From ESP32 GPIO21:

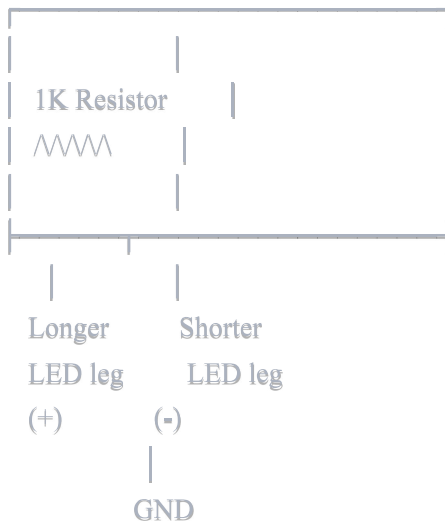


That's it! When GPIO21 goes HIGH, LED lights up.

LED #2: YELLOW (RX Activity)


From ESP32 GPIO8:



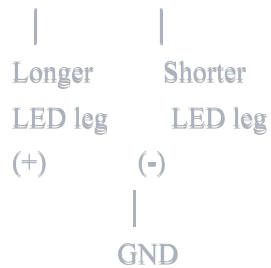

LED #3: RED (TX Activity)

From ESP32 GPIO9:

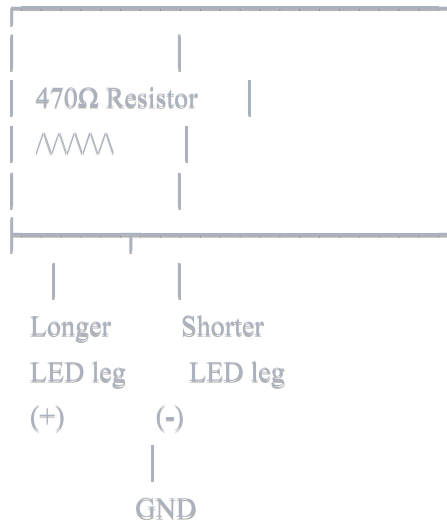

IMPORTANT:


- Long leg of LED = positive (+) goes to resistor
- Short leg of LED = negative (-) goes to GND
- If LED doesn't light, flip it around


PART 3: IR RECEIVER (Photodiode → Meter Data)

PURPOSE: Read infrared signals FROM the meter

STEP 1: Connect Photodiode (WP3DP3BT/BD)

Point this at the meter's IR window:

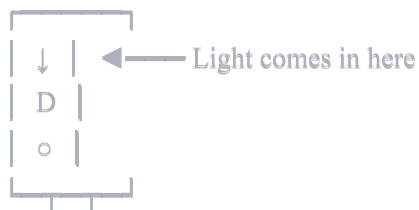

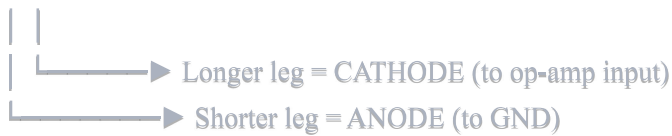

STEP 2: Connect to Op-Amp (OPA2333 - This amplifies tiny signals)

The photodiode puts out TINY currents (picoamps).

The op-amp converts this to readable voltage.

Photodiode cathode (longer leg)




OPA2333 Pinout (8-pin DIP)	
1	Offset Null (leave empty)
2	INPUT (-) ← From photodiode
3	INPUT (+) → to GND
4	GND → Black wire
5	Offset Null (leave empty)
6	OUTPUT → Signal goes out here
7	+3.3V ← Red wire from rail
8	+3.3V ← Red wire from rail

Add 10M resistor + 50pF cap around pins 2 and 6:

(This is the "feedback network" - it sets the gain)

Pin 6 (output)

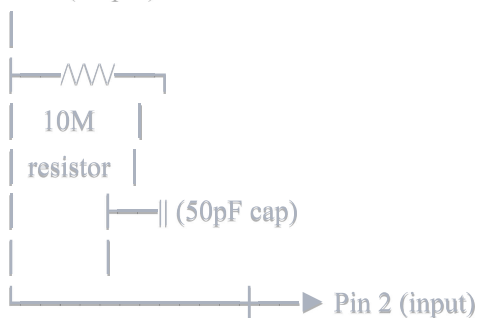

STEP 3: Clean up the signal (Schmitt Trigger)

Use the SECOND half of the same OPA2333:

From first op-amp pin 6 (output)

└─▶ Pin 10 (inverting input)

OPA2333 Pinout (SECOND OP-AMP)

9	—	Offset Null (leave empty)
10	—	INPUT (-) ◀ From op-amp 1
11	—	INPUT (+) ▶ to GND
12	—	GND ▶ Black wire
13	—	Offset Null (leave empty)
14	—	OUTPUT ▶ Clean signal out
15	—	+3.3V ◀ Red wire
16	—	+3.3V ◀ Red wire

Pin 14 output —▶ ESP32 GPIO44 (UART RX input)

SUMMARY OF RECEIVER:

Meter (IR) —▶ Photodiode —▶ Op-amp 1 —▶ Op-amp 2 —▶ ESP32 GPIO44

PART 4: IR TRANSMITTER (Send Signals TO Meter)

PURPOSE: Send infrared signals TO the meter

STEP 1: Connect Optocoupler (TLP291)


This device isolates ESP32 from meter interference.

TLP291 Optocoupler (DIP-4)


Pin 1:	LED Anode (+)
Pin 2:	LED Cathode (-)
Pin 3:	Phototransistor Output
Pin 4:	Phototransistor Emitter

STEP 2: Drive the Optocoupler LED

ESP32 GPIO43 (UART TX)

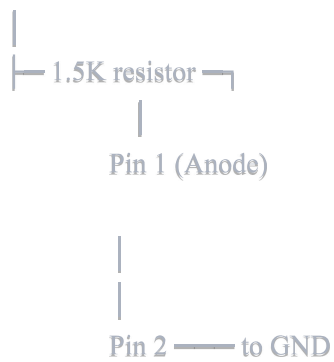

STEP 3: Optocoupler Output drives IR LED

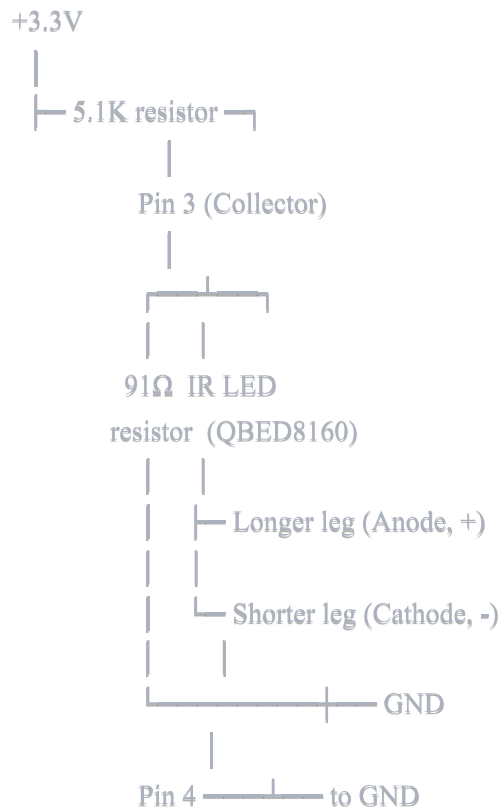

STEP 4: Connections Summary

ESP32 GPIO43 → 1.5K resistor → TLP291 Pin 1
TLP291 Pin 2 → GND
+3.3V → 5.1K resistor → TLP291 Pin 3
TLP291 Pin 3 → 91Ω resistor → IR LED (+)
IR LED (-) → GND
TLP291 Pin 4 → GND

SUMMARY OF TRANSMITTER:

ESP32 GPIO43 → Optocoupler → IR LED → Meter (IR Window)

PART 5: ESP32-S3 BOARD CONNECTIONS

The ESP32-S3 is your brain. Here's what connects where:

ESP32-S3 Development Board	
LEFT SIDE:	RIGHT SIDE:
GND	GND wire (black)
3V3	+3.3V rail (red)
IO43	To optocoupler (1.5K res)
IO44	From Schmitt trigger
IO21	Green LED (1K resistor)
IO8	Yellow LED (470Ω resistor)
IO9	Red LED (470Ω resistor)
USB-C Port (top) = Programming + Debug	

That's it! Only 8 connections to make:

- 1. GND
- 2. 3V3 (+3.3V)
- 3. GPIO43 (to optocoupler)
- 4. GPIO44 (from receiver)
- 5. GPIO21 (green LED)
- 6. GPIO8 (yellow LED)
- 7. GPIO9 (red LED)
- 8. USB-C (for loading code)

COMPLETE WIRING CHECKLIST

Power System:

- ☐ Battery red wire → one side of switch
- ☐ Battery black wire → GND rail
- ☐ Switch other side → AMS1117 VIN
- ☐ AMS1117 GND → GND rail
- ☐ AMS1117 OUT ⇒ +3.3V rail

- ☐ 10 μ F cap on VIN side (+ to VIN, - to GND)
- ☐ 10 μ F cap on OUT side (+ to OUT, - to GND)
- ☐ 100 μ F cap on OUT side (+ to OUT, - to GND)

LEDs:

- ☐ Green LED: GPIO21 — 1K resistor — LED+ (long leg)
- ☐ Green LED: LED- (short leg) — GND
- ☐ Yellow LED: GPIO8 — 470 Ω resistor — LED+ (long leg)
- ☐ Yellow LED: LED- (short leg) — GND
- ☐ Red LED: GPIO9 — 470 Ω resistor — LED+ (long leg)
- ☐ Red LED: LED- (short leg) — GND

IR Receiver:

- ☐ Photodiode cathode (long leg) → OPA2333 pin 2
- ☐ Photodiode anode (short leg) → GND
- ☐ 10M resistor: pin 6 to pin 2 (feedback)
- ☐ 50pF cap: parallel with 10M resistor
- ☐ OPA2333 pins 2,3,4,7,8 wired as shown
- ☐ Second OPA2333 stage: pin 14 → GPIO44

IR Transmitter:


- ☐ GPIO43 — 1.5K resistor — TLP291 pin 1
- ☐ TLP291 pin 2 — GND
- ☐ +3.3V — 5.1K resistor — TLP291 pin 3
- ☐ TLP291 pin 3 — 91 Ω resistor — IR LED +
- ☐ IR LED - — GND
- ☐ TLP291 pin 4 — GND

ESP32-S3:

- ☐ GND to GND rail
- ☐ 3V3 to +3.3V rail
- ☐ GPIO43 to transmitter
- ☐ GPIO44 to receiver
- ☐ GPIO21 to green LED
- ☐ GPIO8 to yellow LED
- ☐ GPIO9 to red LED

Quick Reference: Part Locations on Breadboard

TOP: Power Supply

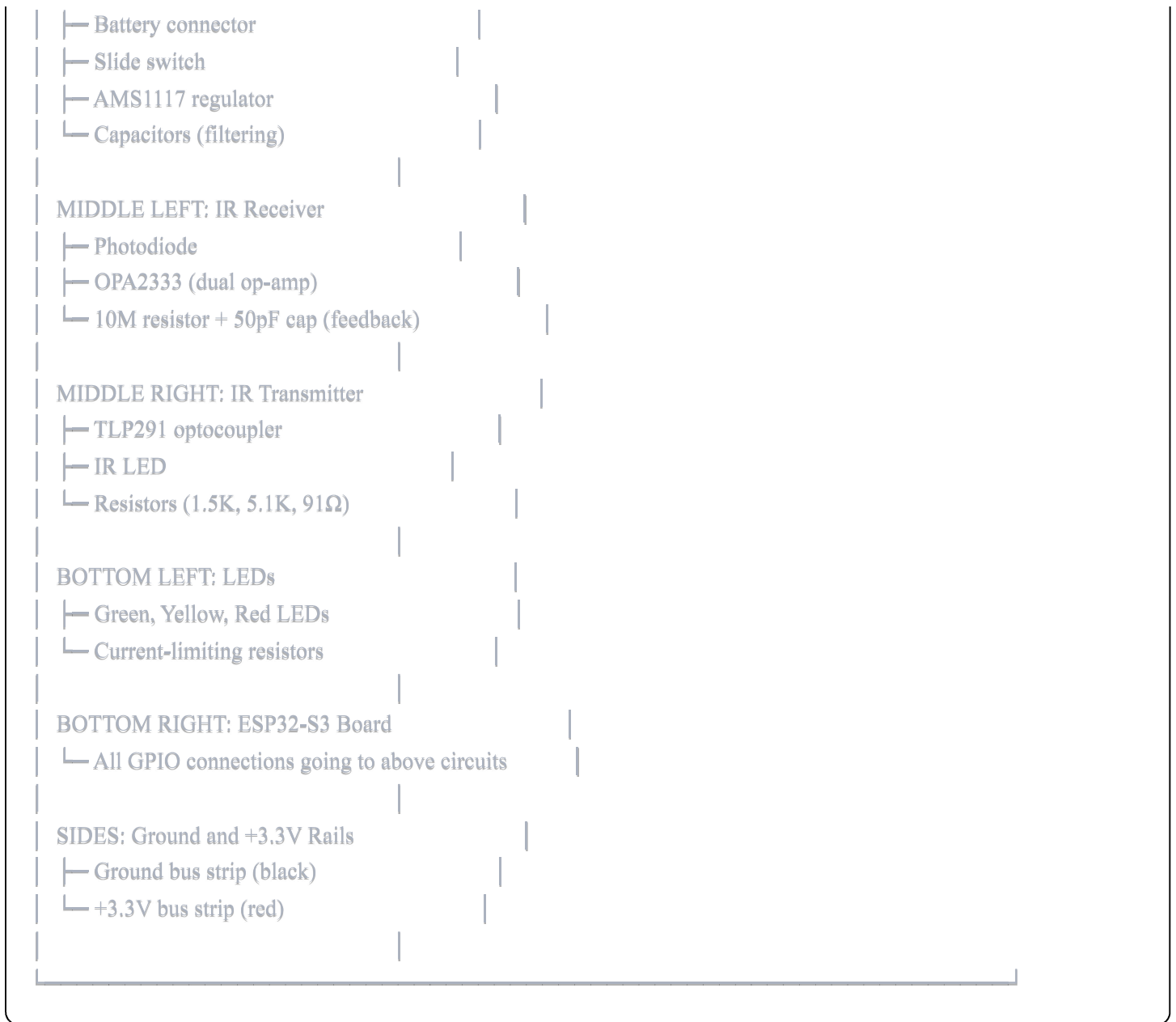

Pro Tips for Building

1. **Start with power first** - Get 3.3V working before adding anything else
2. **Test LEDs early** - They tell you if GPIO is working
3. **Use different colored wires** - Red for +3.3V, Black for GND, Green for signals
4. **Keep short wires** - Long wires pick up noise
5. **Multimeter is your friend** - Test every voltage and connection
6. **Take photos** - Document what you build in case you need to troubleshoot

Good luck! Which part would you like me to clarify further?

